

# IBM<sup>®</sup> Customer Engineering Manual of Instruction

Issued to: J.E. Moss

Branch Office: Atlanta 030

Department: \_\_\_\_\_

Address: \_\_\_\_\_


If this manual is mislaid, please  
return it to the above address

## **60-Cycle SMS Power Supply**



## Contents

INTRODUCTION . . . . .	5
GENERAL DESCRIPTION . . . . .	5
AC REGULATION	
GENERAL . . . . .	7
OPERATION . . . . .	8
AC TO DC CONVERSION	
FULL-WAVE CENTER-TAPPED RECTIFIER . . . . .	9
Circuit Operation . . . . .	9
FULL-WAVE BRIDGE . . . . .	10
Circuit Operation . . . . .	10
BIAS VOLTAGE . . . . .	10
Circuit Operation . . . . .	10
DC REGULATION	
ZENER DIODE . . . . .	11
Temperature Compensation . . . . .	11
THEORETICAL VOLTAGE REGULATOR . . . . .	12
Circuit Operation . . . . .	12
SERIES REGULATOR . . . . .	12
Series Resistor . . . . .	12
DIFFERENTIAL AMPLIFIERS . . . . .	13
Reference to Ground . . . . .	13
Reference to -6 Volts . . . . .	14
EMITTER FOLLOWER AMPLIFIER . . . . .	15
TEMPERATURE COMPENSATION . . . . .	16
CIRCUIT PROTECTION	
ISOLATION TRANSFORMER . . . . .	17
OVERCURRENT . . . . .	17
OVERVOLTAGE . . . . .	17
Thyratron Transistor . . . . .	18
Theoretical Circuit . . . . .	18
OVERVOLTAGE PROTECTION CIRCUIT . . . . .	18
MARGINAL-CHECK UNIT	
MODULATOR UNIT (FIXED) . . . . .	20
Circuit Operation . . . . .	21
PORTABLE UNIT . . . . .	21
Circuit Operation . . . . .	21
TYPICAL DC POWER SUPPLY	
Circuit Description . . . . .	22
TABLE OF AVAILABLE 60-CYCLE SMS POWER SUPPLIES . . . . .	24

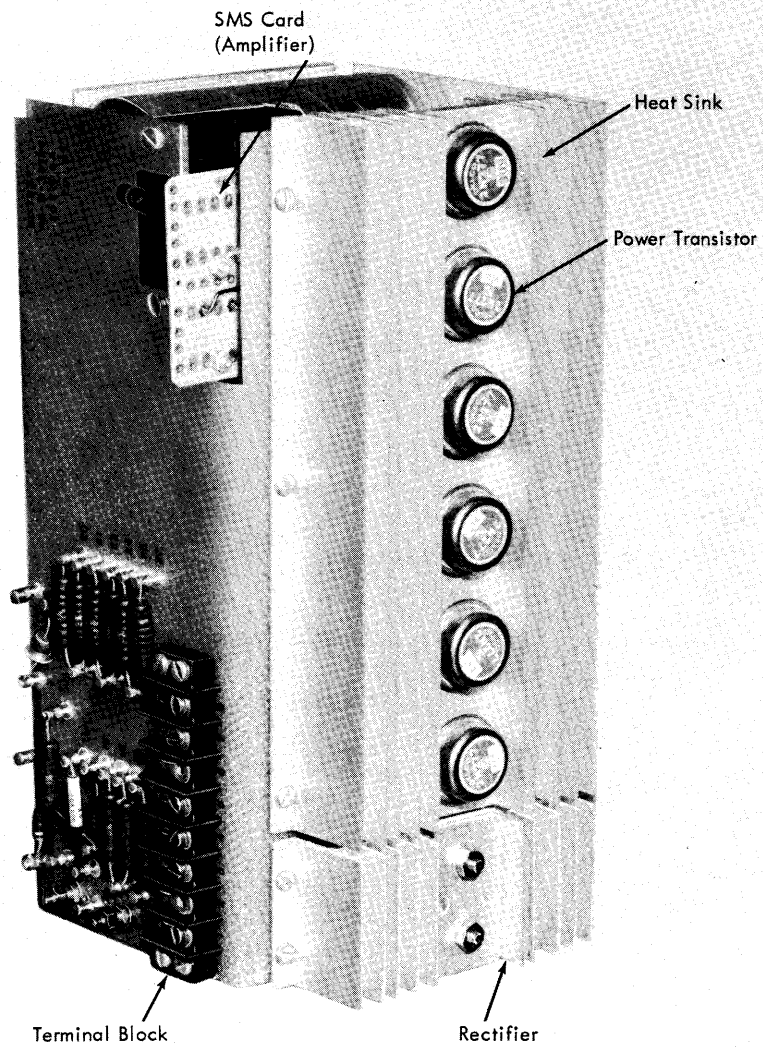

SMS POWER SUPPLY MODULE

## 60-Cycle SMS Power Supply

This manual contains information on the 60 cycle sms power supplies which were designed to provide all the dc voltages required in a solid-state computer. Because these power supplies are used in many different systems and applications, they may be modified to meet an individual need. These variations, not included in this manual, are contained in the manual of instruction on the individual system or machine along with the power-on sequence.

The power supply components are packaged in standard building-block modules. These modules (opposite page) can be mounted in both the Module I (swinging gate) and Module II (sliding gate) type of packag-

ing. At present there are 25 different power-supply modules which satisfy the requirements of most machines. Power-supply systems of different sizes and ratings can be easily designed by using various combinations of the standard power-supply modules available. This eliminates the need of a separate "custom-made" power supply for each system or machine type.

The 1400, 1200, and 1600 series systems use this standard sms power-supply system. The requirements of most machines in the development stages will also be satisfied by these power supplies. (Certain systems, such as the 7070 and 7090, have a 400-cycle power-supply system which will not be discussed in this manual.)

### General Description

Figure 1 shows a power-supply system utilizing these modular units in block form. Each block represents a standard module. The system is described as follows:

The line ac voltage is fed into one or more ferroresonant regulators where it is changed to a regulated ac voltage. This regulated ac voltage is distributed to the dc power-supply modules where it is converted into a regulated dc voltage. The dc voltage is then distributed to the various machine or system circuits requiring it.

The ferroresonant regulators, sometimes referred to as constant-voltage transformers, consist of special transformers and capacitors. The capacitors and the transformers are packaged into separate modules to provide flexibility in mounting. They are located close to each other on the machine.

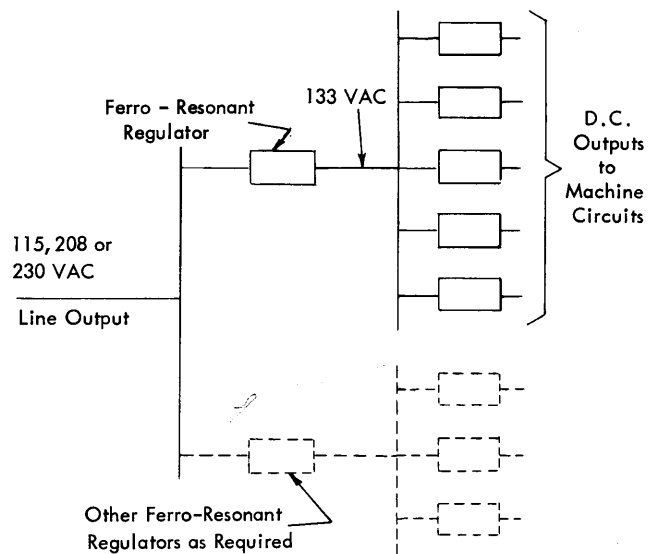


FIGURE 1. TYPICAL SYSTEM DIAGRAM

The dc power-supply module (Figure 2A) consists of an isolation transformer, solid-state rectifiers, associated filter networks, and a magnetic-type circuit breaker for overcurrent protection. The regulation from such a dc power supply is  $\pm 8\%$ , which is sufficient for some applications.

When closer regulation is required, as in most of IBM's transistor circuitry, a dc power-supply module incorporating a series regulator is used. This provides a dc voltage with  $\pm 2\%$  regulation. The series regulator consists of an sms pluggable amplifier card, power transistors, and an additional filter. Overvoltage protection circuits are also provided as required.

Figures 2A and 2B are block diagrams of the standard power supplies.

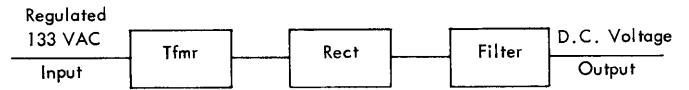


FIGURE 2A. STANDARD POWER SUPPLY

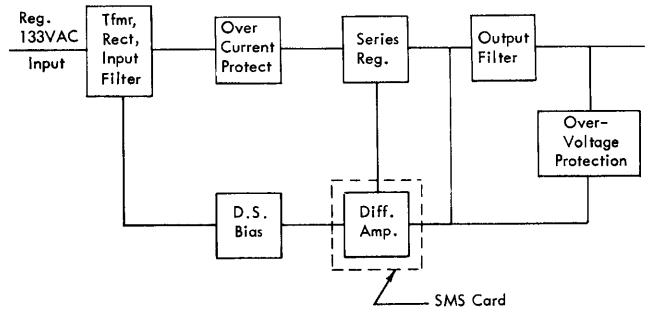


FIGURE 2B. STANDARD SERIES — REGULATED POWER SUPPLY

## AC Regulation

AC regulation is provided by one or more ferroresonant regulators. The ac regulator used in the standard sms power-supply system, described in this manual, changes the line voltage to a regulated voltage of approximately 133 volts ac.

The ferroresonant regulator consists of specially constructed transformers and capacitors. They are available in several output ratings (power) chosen to provide the least number which will satisfy individual machine requirements. Ratings range from 250 to 1840 watts.

The regulator regulates varying line voltages and feeds a constant voltage to the dc power-supply modules, and provides line isolation. This involves the combination of a ferroresonant electrical circuit and a high-leakage magnetic circuit.

Figure 3 shows a typical ferroresonant regulator transformer that is used in standard sms power-supply systems. The electrical circuit consists of two windings: a primary winding, and a secondary winding, which is connected in parallel with a capacitor to form a ferroresonant circuit.

The magnetic circuit is a closed shell-type core equipped with magnetic shunts between the input and output sections. These shunts have air gaps in the flux path as shown.

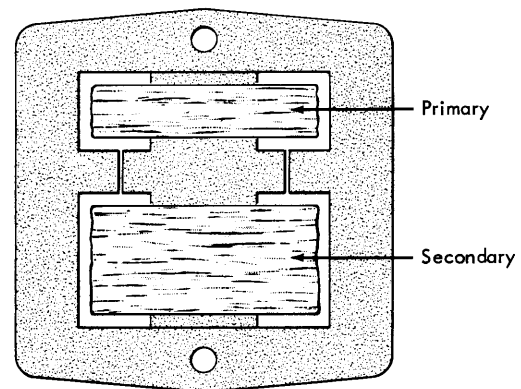


FIGURE 3. FERRORESONANT REGULATOR TRANSFORMER

## Operation

The ferroresonant portion of the transformer consists of the secondary winding and the capacitor shown in Figure 4. It is termed ferroresonant because of ferromagnetic material in the transformer core. A ferromagnetic material has the property of limiting the flux passing through it regardless of how hard the material is driven.

Because of the ferromagnetic properties of a ferroresonant circuit, it has two important properties not displayed by a conventional LC resonant circuit (tank circuit). At a constant input frequency

1. the tank voltage is fixed by the fixed flux change in the ferromagnetic material.
2. the energy in the tank is fixed by the value of the capacitor.

The first of these properties produces the constant output voltage because the output is a portion of the tank voltage. The second property provides the regulating action that takes only enough energy from the primary to supply the energy required by the load, permitting the load to vary.

The action is similar to that of a float valve in an automobile carburetor or a lavatory. A typical float valve is shown in Figure 5A. If the output valve is opened to let water out faster (load current is increased), the tank level will start to drop (energy in the resonant circuit will decrease). As the level drops, the float drops to open the input valve further and maintain the original level.

The action of the float valve in this analogy is accomplished by a phase shift between input voltage and resonant circuit voltage and hence, output voltage. The energy delivered to the tank circuit on each cycle depends on this phase difference. When the output is in phase as shown in Figure 5B, the tank receives little energy. When the output is out of phase as in Figure 5C, it receives a large amount of energy from the primary. Because the resonant circuit maintains a fixed amount of energy, it will shift phase with respect to the primary until it receives exactly as much energy per cycle as the load consumes.

The actual transfer of energy from primary to secondary is accomplished by the magnetic shunt. There is a limit to the energy that can be transferred by a given shunt. Thus, if too heavy a load is placed on the transformer, more energy will be taken out; then the primary can transfer and the output voltage will collapse. The action is similar to opening the output valve completely in the float-valve analogy. If the input cannot supply water fast enough even with the float valve fully open, the water level in the tank drops.

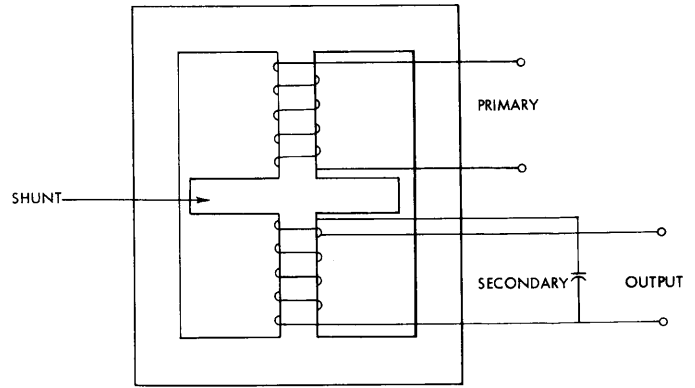


FIGURE 4. FERRORESONANT TRANSFORMER AND CAPACITOR

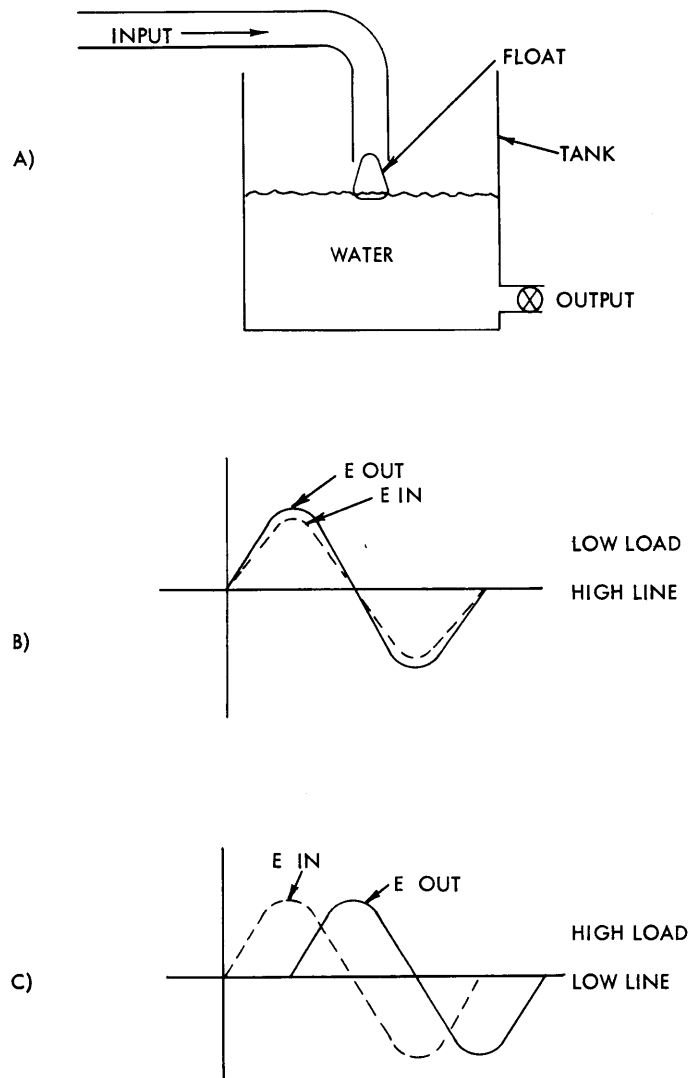


FIGURE 5. FERRORESONANT REGULATING ACTION



## AC to DC Conversion

The regulated ac voltage from the ferroresonant regulator is transformed by an isolation transformer to the correct voltage magnitude and then converted to dc voltage by solid-state rectifiers. Some of the advantages of using an isolation transformer in each module are:

1. One main distribution line (133-volt) from the ferro to each dc power supply.
2. Isolate noise from one dc module to another.
3. A dc power supply may be used for either a negative or a positive voltage.

The sms standard power supplies use two basic rectifier circuits:

1. Full-wave center-tapped
2. Full-wave bridge

### Full-Wave Center-Tapped Rectifier

Figure 6 shows a full-wave center-tapped rectifier circuit similar to those used in sms power supplies rated for less than 20 volts. It is also used in all series regulated sms power supplies, described in this manual, to develop the bias voltage required to operate the regulator transistor circuitry.

#### Circuit Operation

Regulated ac voltage is applied to the primary of T1. The secondary of T1 provides the correct ac voltage to the anodes (arrow heads) of the D1 and D2 silicon diodes.

The e1 and e2 voltages are developed across the two halves of the secondary, with respect to the center tap, as noted in Figure 6. The e1 and e2 voltages are of equal magnitude and  $180^\circ$  out of phase with each other.

Electron flow from the center tap (point B) through R1 and D1, and the upper half of T1 results in a positive voltage pulse across R1.

The anode of D1 is positive with respect to the center tap at time 1 (t1) of the first cycle shown. (Note that the anode of D2 is negative at this time.)

During the following half cycle (t2), the polarity of the voltages developed across the two halves of T1 is reversed. The anode of D2 is now positive, while the anode of D1 is negative with respect to the center tap. Electron flow from the center tap through R1, D2 and the lower half of T1 also results in a positive pulse being developed across R1. Alternate conduction through D1 and D2 results in a pulsating dc output voltage being developed across R1.

If added to the circuit, capacitor C1 would serve as a filter and smooth out the pulsating dc voltage waveform as illustrated in Figure 6.

D1 and D2 are silicon diodes about the size of a sewing thimble known for their ability to pass large currents.

Full-wave rectification utilizes the full cycle of the input voltage; therefore, the output pulsations (ripple) are twice the frequency of the input voltage.

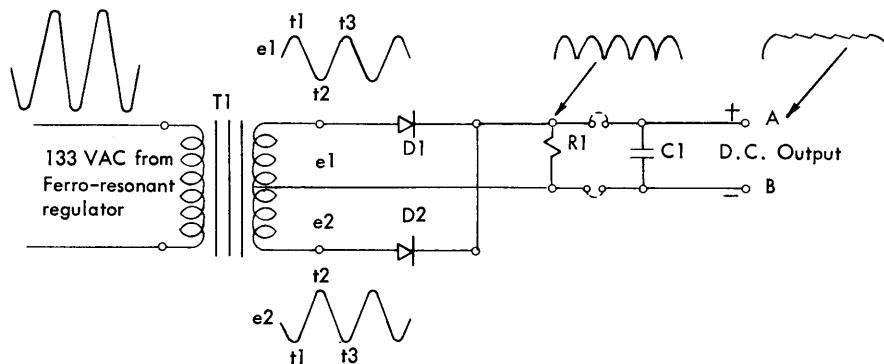


FIGURE 6. FULL-WAVE CENTER-TAPPED RECTIFIER CIRCUIT

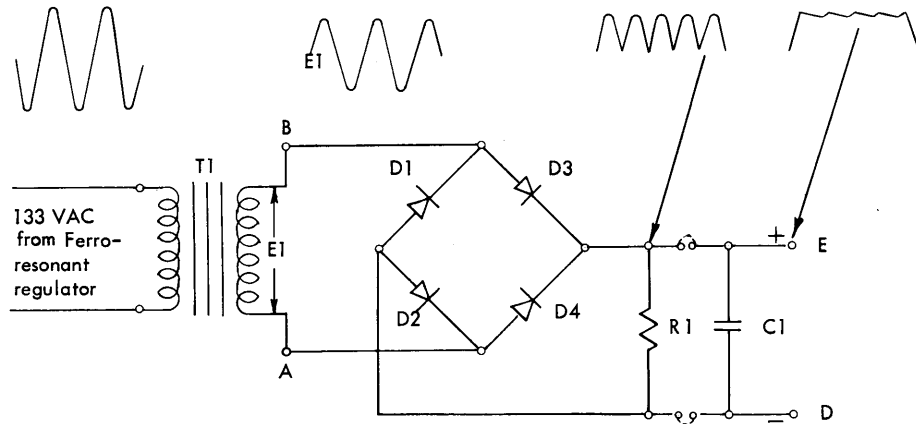


FIGURE 7. BRIDGE-TYPE FULL-WAVE RECTIFIER CIRCUIT

### Full-Wave Bridge

The full-wave bridge-type rectifier circuit is used in most standard SMS power supplies rated at 20 volts dc or more. The 20-volt, 6-amp power supply, which uses a center-tapped full-wave rectifier circuit, is an exception.

Figure 7 shows a typical bridge-type rectifier circuit. The two major differences between this type rectifier circuit and the center-tapped rectifier circuit previously described are:

1. Four silicon diodes are used instead of two.
2. The entire secondary voltage, rather than one half of it, is utilized on each half cycle.

#### Circuit Operation

With a regulated ac input to the primary of T1, a stepped-down ac voltage of correct magnitude is developed across the secondary. When the top of the secondary is positive with respect to the bottom of the secondary winding, the electron flow starts with the negative output terminal, point D, through R1, D3, the secondary winding of T1, through D2, back to point D. On the alternate half cycle, when the bottom of the secondary is positive with respect to the top half of the secondary winding, the electron flow starts at point D, through R1, D4, the secondary winding of T1, through D1, back to point D.

The electron flow was through R1 from the negative terminal to the positive terminal in each case. This develops a pulsating dc voltage across R1 as shown by the waveform in Figure 7.

The capacitor action is the same as in the full-wave rectifier circuit previously described. It tends to smooth out the pulsations as shown in Figure 7, when connected to the circuit.

Bridge-type rectifier circuits utilize the full cycle of the input voltage; therefore, the ripple frequency is twice that of the input voltage frequency. The full voltage existing across the entire secondary winding is rectified with a bridge-type rectifier; therefore, the output voltage is twice that of a center-tapped full-wave rectifier which rectifies one half of the secondary voltage at a time.

### Bias Voltage

Each dc power supply module incorporating a series regulator has two rectifier circuits:

1. the main rectifier circuit which is used to develop the output voltage,
2. another rectifier circuit in the bias supply which develops the voltage required by the series regulator circuitry.

The bias supply consists of two solid-state diodes and filter capacitance. The diodes are connected, as a full-wave center-tapped rectifier circuit, across an additional secondary winding of the isolation transformer. It develops approximately 30 volts dc.

#### Circuit Operation

See *Circuit Operation, Full-Wave Center-Tapped Rectifier*.

## DC Regulation

Regulation for ac input voltage variations is primarily provided by the ferroresonant regulator. Additional regulation for input voltage variations and regulation for load variations are provided by a series regulator.

The series regulator incorporates the following units:

1. A zener diode for reference voltage.
2. Series regulator transistors.
3. A differential amplifier.
4. A two-stage emitter-follower amplifier.
5. A separate dc voltage supply to bias the transistor circuitry.

The zener diode, differential amplifier, and two-stage emitter-follower amplifier are mounted on an SMS card. The series regulator transistors are mounted on a large piece of metal, called a *heat sink*, which forms one side of the dc power-supply module as shown in the frontispiece.

One type of differential amplifier card is used for all dc power-supply modules referenced to ground. Power supplies referenced to  $-6$ , such as certain  $-12$  volt supplies, require a different pluggable amplifier card.

### Zener Diode

The zener diode is a solid-state device constructed with a constant reverse bias breakdown voltage. At this breakdown voltage, called zener breakdown voltage, the current through the diode is limited only by the impedance of the circuit in which it is used.

Zener breakdown always occurs at the same voltage for a given type of zener diode. Because the voltage drop across a zener diode is practically constant (zener breakdown) over a wide current range, this component can be used as a voltage reference device. Circuit-wise, it may be compared to a gas type voltage regulator tube (Figure 8A).

Notice that when the applied voltage drops (Figure 8B), the entire change is reflected across the resistor and the voltage across the zener diode remains constant at 10 volts.

The zener diode used in the SMS power supply described in this manual develops a constant voltage of 10 volts which is used by a differential amplifier as a standard voltage. A sample of the rectified output voltage is also fed to the differential amplifier where it is compared against the standard 10 volts. The output of the differential amplifier is used to maintain the correct output voltage.

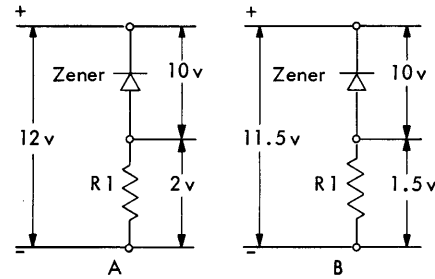


FIGURE 8. CONSTANT VOLTAGE ACTION, ZENER DIODE

### Temperature Compensation

The zener breakdown voltage increases as the temperature rises. This is an undesirable characteristic because the zener breakdown voltage is used as a standard for comparison as previously mentioned. A forward-biased conventional diode, which reacts to temperature changes in the opposite manner, is used in series with the zener diode (Figure 9) to form a temperature-compensated device.

Assume that a temperature increase raises the zener voltage drop across the zener diode to 9.7 volts. Simultaneously, the increased temperature decreases the voltage across the conventional diode to .3 volt. The reference voltage remains unchanged at 10 volts.

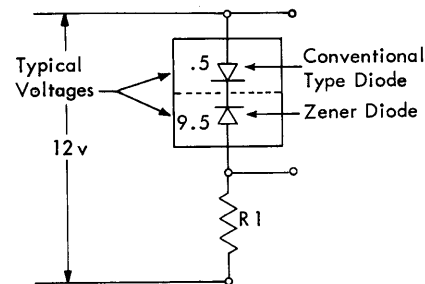


FIGURE 9. TEMPERATURE-COMPENSATED ZENER

## Series Regulator

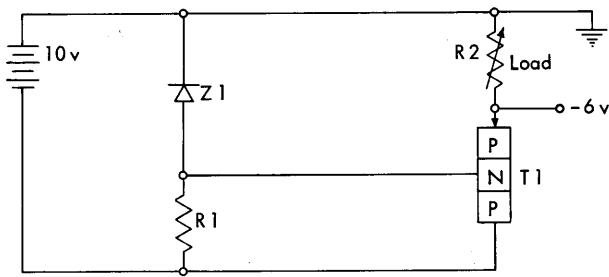


FIGURE 10. THEORETICAL VOLTAGE REGULATOR CIRCUIT

### Theoretical Voltage Regulator

Figure 10 shows a circuit in which a 6.2 volt zener diode is used as a voltage reference device. The variable resistor R2 represents the load resistance. The battery represents a rectifier.

The zener diode (Z1) provides a fixed voltage of -6.2 volts on the base of the regulator transistor (T1). The load (R2) is in the emitter circuit of T1, and together they form a simple emitter follower circuit. Any change in the R2 load which tends to change the voltage drop across it, causes T1 to conduct more or less to keep its emitter potential at -6 volts. The emitter potential in an emitter follower circuit tends to follow the base potential.

#### Circuit Operation

Let a decrease in the load resistance (R2) lower the voltage drop across it. This changes the base to emitter potential and causes increased current to flow through the transistor. The increased current flow through R2 raises the voltage across it.

Any change in the emitter voltage, because of changes in the load resistance, is countered by a change in the emitter - base potential. It is this action that causes Z1 and T1 to act as a voltage regulator.

Voltage regulation in the standard SMS power supplies is accomplished in a similar manner.

The series regulator controls the output voltage of the power supply. It is controlled by the output of an amplifier and consists of one or more paralleled power transistors in series with the negative terminal of the rectifier section and the negative output terminal of the power supply.

The simplified diagram in Figure 11 shows a series regulator and its relationship to the power supply. The number of power transistors in parallel depends upon the current and voltage rating of the power supply. (For example, four transistors are used for 8 amps on a 12 volt power supply, while only three are required for 8 amps in the 6 volt power supply.)

To have conduction in the transistor, there must be a difference of potential across it; therefore, the rectifier circuit must develop a voltage higher than that required at the output terminals of the power supply. This is usually about 3 volts greater than the rated output voltage of the power supply.

The rate of conduction through the power transistor is dependent upon its base to emitter potential. If the base swings positive with respect to the emitter, the current flow decreases. If the base voltage swings negative with respect to the emitter, the current through the transistor increases. By regulating the current flow through the load, we maintain the rated output voltage. In  $E = IR$ , R is the load.

#### Series Resistor

The two resistors in series with the emitters of the power transistors in Figure 11 balance the current through the transistors when more than one transistor is used. They are .2 ohm 5-watt precision resistors and are called series resistors.

Consider the power transistor a variable resistor. Its resistance changes as the base to emitter voltage changes. In other words, if the base goes positive with respect to the emitter, the resistance increases. Saying the same thing another way, if the emitter becomes negative with respect to the base, the resistance of the power transistor increases.

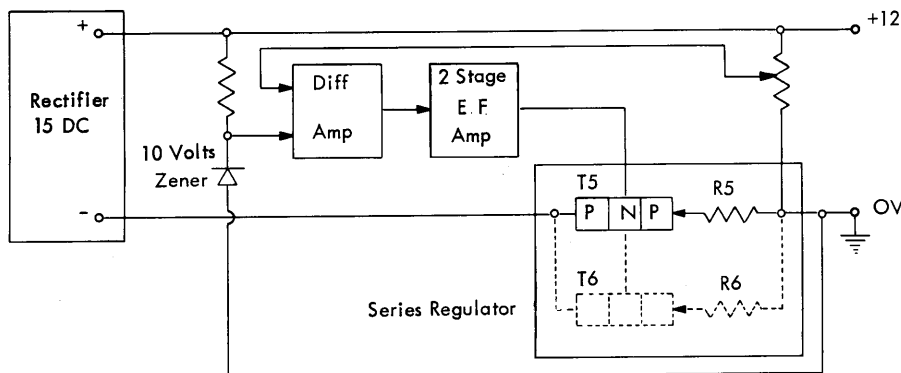


FIGURE 11. SERIES REGULATOR TRANSISTORS

The bases of both power transistors are tied together in Figure 11. If T5 started to conduct more than T6, the increased voltage drop across R5 would make the emitter of T5 slightly more negative than the emitter of T6. This action increases the effective resistance of T5. If the effective resistance of T6 remains constant and the resistance of T5 becomes greater, T6 will conduct more. This action continues until the current flow is evenly balanced between the two transistors.

## Differential Amplifiers

### Referenced to Ground

As stated previously, there are two types of differential amplifier pluggable cards (sms cards):

1. the card that is used for dc power-supply regulators referenced to ground
2. the card that is used with regulators in the dc power-supply modules referenced to -6 volts.

A dc power-supply module referenced to ground is one that has its regulation tolerance specified in relation to ground potential. For example, a 12-volt power supply referenced to ground with a regulation tolerance of  $\pm 2\%$  should maintain an output voltage of between 11.76 and 12.24 volts.

Although the same sms card is used in all dc power-supply modules that are referenced to ground, that part of the regulator circuitry not mounted on the sms card may vary from one dc power-supply module to another. The differential amplifier circuitry for power-supply modules referenced to ground can be broken into two basic circuits:

1. the circuit used in 6-volt power-supply modules
2. the circuit used in all other series-regulated power-supply modules.

## 6-VOLT POWER SUPPLIES

Figure 12 is a simplified diagram of the differential amplifier used in 6-volt power supplies. The -30-volt bias is developed by a separate rectifier circuit within this power-supply module. The 10-volt zener diode keeps the voltage across R1 constant at 10 volts. The potentiometer is set to about -6 volts with respect to ground which is the positive terminal in this example. Because T1, together with R3, forms an emitter follower circuit, its emitter is fixed to a definite potential in reference to ground (about -6 volts). The emitter of T2, which is common to the emitter of T1, has a fixed voltage in reference to ground (about -6 volts). The base of T2 is connected to the negative output line of the power supply.

**Circuit Operation** - The objective is to recognize any change in the output voltage level and signal, through an amplifier, the series regulator so that it can maintain the specified voltage output level. This signal comes from the collector of T2.

Normally, with -6 volts output, the base potential of both T1 and T2 is the same. Both T1 and T2 share the current flow through R3 to maintain a 6-volt drop across R3. This provides a certain potential at the collector of T2, which, through an amplifier, signals the series regulator to maintain its present rate of conduction.

If the external load on the power supply should suddenly change and cause the output voltage to decrease, the base of T2 tends to change in a positive direction, in reference to its emitter which is clamped -6 volts. This action turns T2 off (decrease the current flow) which causes the collector of T2 to become more negative. The negative swing in collector voltage at T2 causes an increase in the rate of conduction through the series regulator transistors which raises the output voltage level.

If the output voltage should increase (go more negative), T2 would turn on more and cause the collector voltage of T2 to change in a positive direction. The positive swing causes the series regulator transistors to turn off (conduct less), which lowers the output voltage.

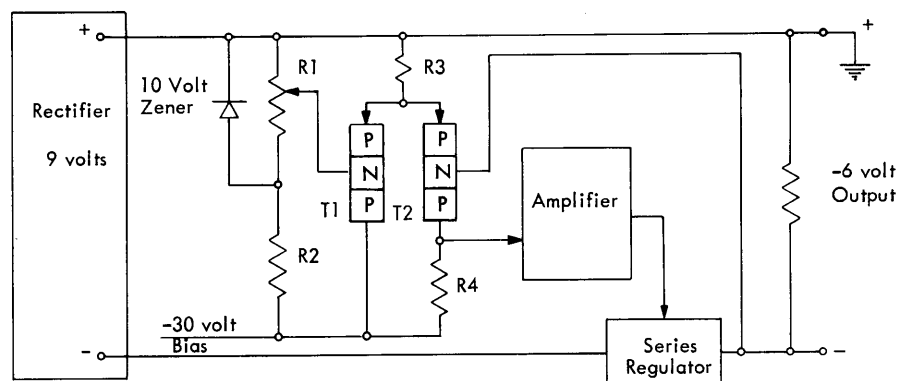


FIGURE 12. DIFFERENTIAL AMPLIFIER FOR 6-VOLT POWER SUPPLIES

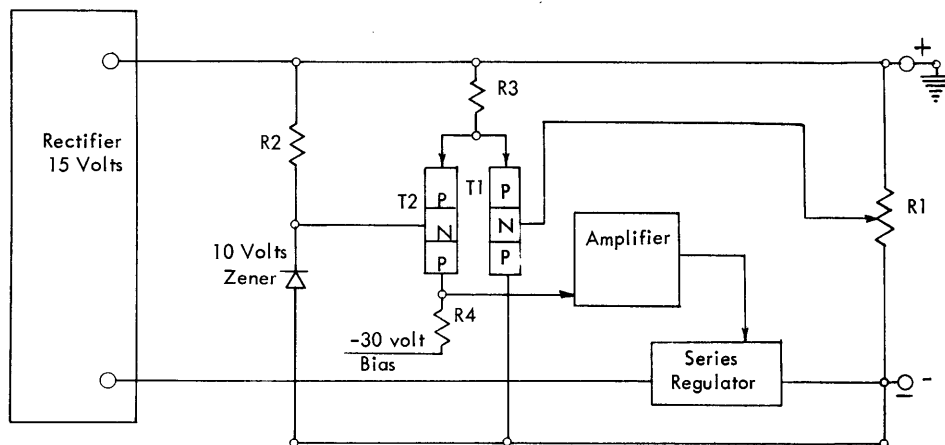


FIGURE 13. DIFFERENTIAL AMPLIFIER FOR 12-VOLT OR MORE POWER SUPPLIES

#### 12-VOLT OR MORE POWER SUPPLIES

The differential amplifier circuit in Figure 13 is used in the standard SMS power supplies that are referenced to ground and rated for 12 volts or more. It is similar to the differential amplifier previously discussed for 6-volt power supplies and incorporates the same SMS card.

Assume that the positive output terminal of the supply is connected to ground. The base of T1, which is an emitter follower, is set to about -2 volts with respect to ground. This clamps the emitter of T2 to about -2 volts. Notice that this voltage will vary simultaneously with a change in the output voltage. The base of T2 is connected to a zener developed voltage which is ten volts more positive than the negative output voltage (-2 volts under no load conditions). Any variation in the output voltage changes the base to emitter voltage of T2. This action varies the collector potential of T2 which controls the conduction through the series regulators to maintain the specified output voltage.

*Circuit Operation* - If the output voltage should increase to -12.2 volts, for example, the base potential of T2 will go more negative (from -2 volts to -2.2 volts). This action causes T2 to turn on more, which results in its collector potential becoming more positive. The series regulator transistors, sensing this change, tends to turn off, lowering the output voltage.

Notice that when the output voltage increased, the entire amount of change was reflected on the base of T2, while only a portion of the change was reflected onto the base of T1 because of the voltage divider action of R1.

If the output voltage drops from -12 volts to -11.8 volts, for example, the base potential of T2 becomes more positive with respect to ground which causes T2 to turn off. This action makes the collector voltage of T2 more negative, which causes the series regulator to turn on more. The increased current flow raises the output voltage.

#### Referenced to -6 Volts

Certain transistor applications require a tighter tolerance between -12 volts and -6 volts than is provided for with the normal differential amplifier circuit. To satisfy this requirement, a scheme using -6 volts as the regulating voltage is incorporated. Minus twelve-volt power supplies that might require this type regulation may be referenced to either -6 volts or ground by using the proper SMS differential amplifier card.

Normal regulation of  $\pm 2\%$  in reference to ground results in the following permissible voltages:

For -6 volt supplies: between -5.88 and -6.12 volts

For -12 volt supplies: between -11.76 and -12.24 volts

Notice that if the -6-volt supply is at -5.88 volts and the -12-volt supply is at -12.24 volts, a difference of 6.36 volts between the two supplies exists. In other words, while the two supplies are regulated to a tolerance of  $\pm 2\%$ , the difference between the two voltages can vary up to  $\pm 6\%$ . This variation would cause erratic operation in some transistor applications.

By using the -6-volt supply as a reference voltage, and regulating the -12-volt power supply against it instead of ground, a tolerance of  $\pm 2\%$  of the difference voltage can be maintained between these two voltages.

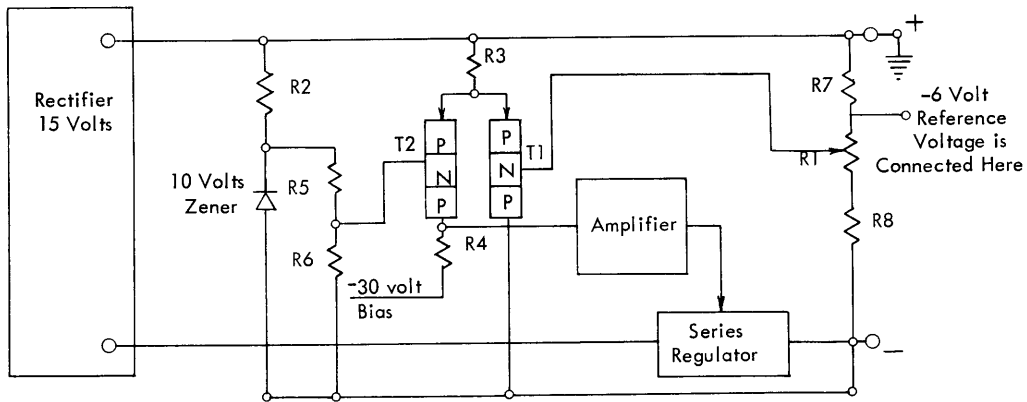


FIGURE 14. DIFFERENTIAL AMPLIFIER FOR POWER SUPPLIES REFERENCED TO -6 VOLTS

Figure 14 shows a simplified circuit diagram of the differential amplifier used in power supplies referenced to -6 volts. Notice that the output from the -6-volt supply is connected between potentiometer R1 and ground (the positive terminal in the example). This takes R7 out of the circuit and causes the base potential of T1 to vary in step with the -6-volt supply instead of ground. The zener diode develops a constant 10-volt drop across R5 and R6. Any change in the voltage across R1 and R8 will change the rate of conduction in T2 which controls the series regulator transistors. Therefore, the -12-volt output will regulate to a tolerance of  $\pm 2\%$  of the 6-volt difference with respect to the -6-volt power supply.

*Circuit Operation* - The circuit operation is the same as that previously described for differential amplifiers in the power supplies referenced to ground.

### Emitter Follower Amplifier

The simplified circuit diagram in Figure 15 shows the two stages of amplification following the output of T2 in the differential amplifier circuit. It is an emitter-follower circuit and provides sufficient current to drive the power transistor (s) in the series regulator.

An emitter follower is a current-amplifying device, not a voltage amplifier; therefore, approximately the same voltage change appears at the emitter of T4 as on the collector of T2. This current had to be amplified because the series regulator transistors require much more current to control the output than is available from T2. The current gain for each stage of amplification is between 20 and 100.

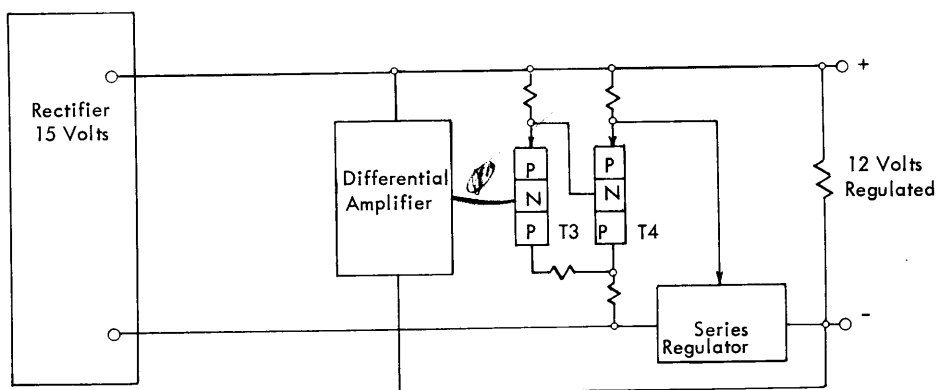


FIGURE 15. TWO-STAGE EMITTER FOLLOWER AMPLIFIER

## Temperature Compensation

The two-transistor-differential amplifier compensates for the increased conduction in a transistor caused by heat.

As the temperature increases, T1, which forms a simple emitter-follower circuit as shown in Figure 16, conducts heavier. The increased conduction, which is through R1, causes a larger voltage to be developed across the emitter resistor. The increased voltage drop across R1 decreases the base to emitter potential of T2. This action tends to turn off T2, opposing the turn-on effect of the increased temperature.

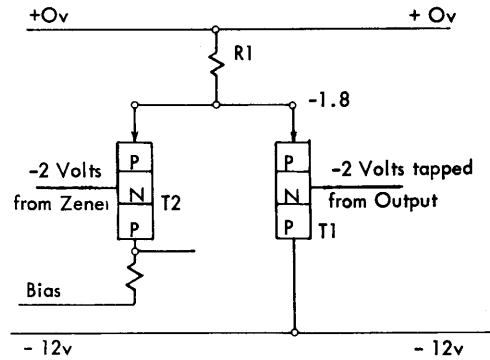


FIGURE 16. TEMPERATURE COMPENSATION



### Isolation Transformer

Protection to the isolation transformer, in the event of a power supply component failure, is provided by means of a circuit breaker in series with the primary winding of the isolation transformer. It is physically located near the overcurrent circuit breaker. This is a thermal-type circuit breaker incorporating a bi-metallic element. It operates two sets of contacts:

1. a normally closed contact in series with the primary winding of the isolation transformer and,
2. a normally open set of contacts which may be used for external purposes.

The contacts may be manually operated by means of the reset plunger, which resets the circuit breaker. The plunger has a white ring around its base which is exposed when the circuit breaker is operated. This indicates to the customer engineer that the circuit breaker is open.

### Overcurrent

Overcurrent protection up to and including a short circuit is provided, by means of a circuit breaker, to protect power-supply components on most SMS power

supplies. Figure 17 shows a circuit breaker connected in a power-supply module. It is in series with the negative output terminal of the rectifier section and the series regulator transistors. In addition to controlling normally closed contacts which are in series with the negative output line, the circuit breaker controls another set of points used for external functions, such as stopping the machine and indicating the trouble.

The circuit breaker is designed to trip in approximately 40 ms at 150% overload. Once tripped, it must be manually reset by a customer engineer. The front-piece shows where it is located on the dc power-supply module.

### Overvoltage

Overvoltage protection is provided, when necessary, for protection of the machine circuitry. Whenever the voltage rises more than 10% above its rated value, the overvoltage protection circuit overloads the power supply, causing the overcurrent circuit breaker to trip.

The overvoltage protection unit includes a zener (for reference voltage), a differential amplifier, and a gate-controlled solid-state rectifier, sometimes called a *thyatron transistor*. It takes about 10 microseconds to react to an overvoltage condition.

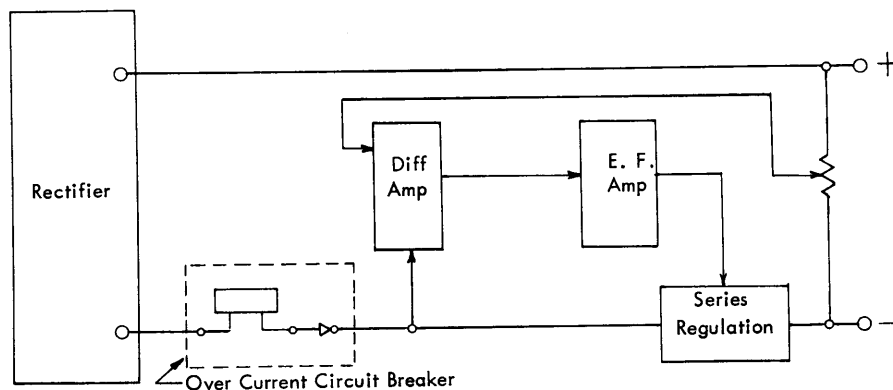


FIGURE 17. OVERCURRENT CIRCUIT PROTECTION

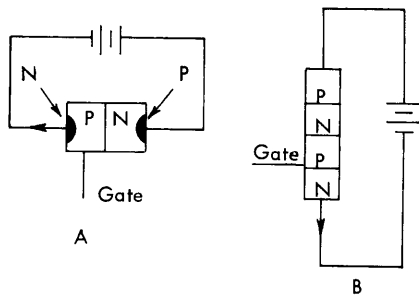


FIGURE 18. THYRATRON TRANSISTOR

### Thyatron Transistor

The thyatron transistor (gate-controlled solid-state rectifier) is a four-element device with characteristics similar to those of a gas rectifier. As in the gas rectifier, there are two operating conditions:

1. in the OFF (nonconducting) state, only leakage current flows.
2. in the ON state, current is limited only by the external circuit impedance. The voltage drop across the transistor in the ON state is about equal to that of one forward-biased PN type rectifier.

The thyatron transistor (PNPN) is constructed by diffusing two layers of P-type material to an N-type silicon wafer. An N-type emitter is diffused on one of the layers of P material, and a gate lead is attached to the same layer of P material. Figures 18A and 18B illustrate a PNP thyatron transistor.

Because of its electrical properties, the thyatron transistor stays in its ON state once it is turned on. The collector voltage necessary to turn it on depends upon the potential applied to the gate lead. If the gate lead is positive with respect to the emitter, the thyatron transistor turns on with a relatively small collector voltage.

### Theoretical Circuit

The theoretical circuit (Figure 19) uses a zener diode and a thyatron transistor. The gate of the thyatron transistor (T1) becomes positive, with respect to its emitter, when the output voltage exceeds  $-6.2$  volts. This is due to the clamping action of the zener diode. When T1 turns on, it acts as a short circuit across the output of the power supply, which trips the overcurrent circuit breaker previously described.

Once the transistor is in conduction, the gate lead loses control. The only way the transistor can be turned off is to open the emitter circuit, which is done by a set

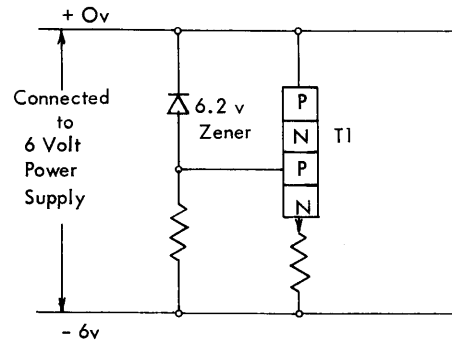


FIGURE 19. THEORETICAL OVERVOLTAGE PROTECTION CIRCUIT

of normally closed points on the overcurrent circuit breaker.

### Overvoltage Protection Circuit

Figure 20 is a typical circuit diagram of the overvoltage protection unit used with a 12-volt power supply. The voltages shown are approximate values.

The overvoltage circuit has two conditions:

1. the condition for normal power supply output;
2. the state it is in to cause the thyatron transistor to turn on.

The circuit description for each will be discussed separately.

#### NORMAL CONDITION

The zener diode (Z1) clamps the emitter of T2 to  $-6$  volts because of the emitter follower action of T1. The collector potential of T2 is set at  $-15$  volts by the potentiometer (R1). Because its base is more negative than its emitter (NPN), T3, which is turned off, acts as an open circuit and keeps the gate potential of T4, the same as its emitter ( $-12$  volts). This keeps T4 in its OFF state.

#### OVERVOLTAGE CONDITION

An increase in the power-supply output raises the voltage across the R1, R2 voltage-divider circuit. This increases the base potential of T2 (becomes more negative) and causes the transistor to turn on more. The base voltage of T3 drops (goes from  $-15$  to less than  $-12$  volts), and T3 turns on. The path of current flow is through R3, R4, T3 to the zero-volt line. This action causes a voltage drop across R3 which makes the gate of T4 positive with respect to its emitter. T4 turns on and acts as an overload to the power supply causing the overcurrent circuit breaker in the power supply to trip.

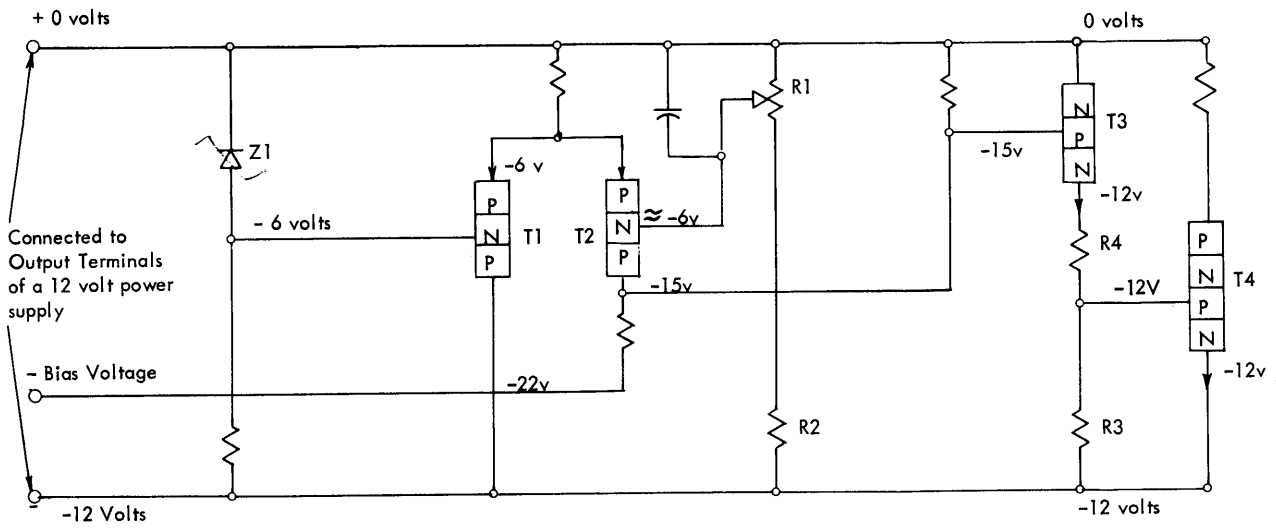


FIGURE 20. OVERVOLTAGE PROTECTION UNIT CIRCUIT

## Marginal-Check Unit

A marginal-check system will be furnished for most systems or machines incorporating solid-state circuitry. The system consists of a special power supply with a variable output voltage which, when placed in series with one of the standard system or machine power supplies, assists the customer engineer in locating marginal or intermittent failures.

The marginal-check power-supply system covered in this manual has two basic designs: one suitable for mounting in an SMS gate and the other, a portable unit, not suitable for SMS mounting. Both units operate in the same manner. The principal difference is that the SMS mountable unit uses the machines ferroresonant regulator for its ac regulation, while the portable supply contains its own.

Both supplies vary the voltages furnished to transistor base circuits. They supply a variable  $\pm 3$  volts at 5 amps. This permits the customer engineer to change a particular voltage by  $\pm 3$  volts, if necessary. For example, a  $-12$ -volt line can be varied from  $-9$  volts to  $-15$  volts.

The scheme used in various systems or machine types to connect the marginal-check supply voltage to a specific voltage will be discussed in the manual of instruction for that particular machine type. Some systems, such as the 1401, will incorporate a set of push buttons, while others might use switches or slotted jumpers on a terminal board.

## Modular Unit (Fixed)

The marginal-check unit designed to fit in an SMS gate is used on machines or systems that have available space and are of sufficient size to justify the costs of the unit.

The output voltage is controlled by a rheostat-switching assembly. With the rheostat in its center position, the output voltage is zero. The output voltage increases from zero to a maximum of 3 volts, either plus or minus, depending upon the direction of rotation as the rheostat is rotated from its central or neutral position.

Figure 21 is the wiring diagram for the marginal-check power supply composed of the following components:

1. An autotransformer
2. An isolation transformer.
3. A full-wave rectifier with a capacitor-inductance filter
4. A polarity reversing relay assembly
5. A rheostat assembly

The rheostat and autotransformer are ganged together and have a switch actuating cam on the end of their operating shaft which controls the polarity reversing relay.

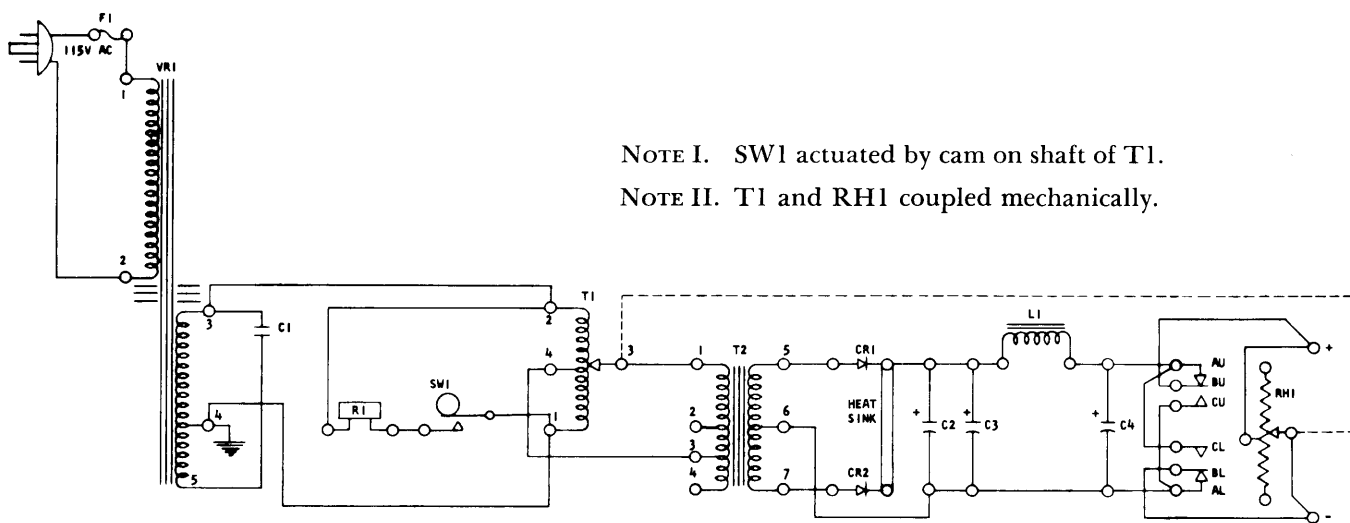


FIGURE 21. MARGINAL-CHECK POWER SUPPLY (PORTABLE UNIT)

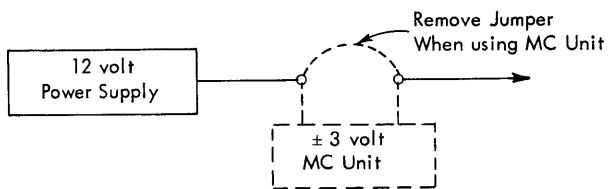


FIGURE 22. MARGINAL-CHECK UNIT IN SERIES WITH SMS POWER SUPPLY

### *Circuit Operation*

With the rheostat in its neutral position (Figure 21) the autotransformer (T1) is also in its center position which means that the voltage across the isolation transformer (T2) is zero. If the unit is connected in series with a system power supply as shown in Figure 22, the rheostat acts as a short circuit and the marginal-check unit has no effect on the machine power supply.

As the rheostat is rotated, the ganged autotransformer also rotates. A voltage is induced in transformer T2 which is rectified. The rectified dc voltage across RH1 acts like a battery in series with a power supply and either adds to or subtracts from the voltage that it is in series with. The amount of voltage across RH1 depends upon the amount of voltage supplied to the rectifier by the autotransformer.

Switch SW1 is actuated by a cam connected to the rheostat autotransformer shaft, as previously mentioned, and is operated when the rheostat is operated from its neutral position in a counterclockwise direction. When closed, the switch operates relay R1, which reverses the polarity of the output voltage.

For a circuit description of the rectifier section, refer to the section in this manual on Full-Wave Center-Tapped Rectifier.

### **Portable Unit**

The portable marginal-check unit is designed for small and intermediate size machines that do not have available space or which cannot economically justify a fixed unit. Because the unit is portable, it can be used on many different machines like the portable dynamic timer power pack.

The unit operates on 115 volts ac and has a ferro-resonant regulator built into it. In all other respects, it is the same as the fixed marginal-check unit previously described.

### *Circuit Operation*

See circuit operation for the fixed marginal-check unit.

## Typical DC Power Supply

The wiring diagram (Figure 23) is for a 6-volt 2-amp sms power supply. The circuit is drawn as it will appear in the wiring diagrams furnished with the machines. This particular power supply was chosen because it is representative of most standard 60-cycle sms power supplies incorporating a series regulator. The shaded lines and circled numbers are added to make the circuit description easier.

Description by section numbers:

1. Isolation transformer.
2. Isolation transformer protection circuit breaker, extra set of points (CB2 AUX) used externally.
3. Bias voltage rectifiers and filter. Furnishes  $-30$  volts for regulator circuitry.
4. Output voltage rectifiers and filter. Provides dc output voltage. Develops a voltage approximately 3 volts higher than the rated output voltage of unit.
5. Overcurrent circuit breaker. Protects power-supply from overload. In series with the negative output line.
6. Series regulator transistor. In series with negative output line.
7. Two-stage emitter-follower amplifier (output taken from emitter of X4 and connected directly to base of X5, section 6).
8. Differential amplifier. Output from X2 connects to base of X3, section 7.
9. Zener diode and voltage divider network. Zener keeps voltage drop across R4, R11, R3 combination constant.
10. Output terminals (TB1-7 and TB1-6) and an additional filter (C2 and R13).
11. Overvoltage protection unit receptacle. If overvoltage protection is specified, the protection unit will be plugged into this receptacle; otherwise, these terminals remain dead-ends.

### *Circuit Description*

Because the individual circuits are explained in other sections of this manual, this circuit description will be confined to two objectives:

1. From the negative side of the filter capacitor at the rectifiers to the negative output terminal.
2. From the positive terminal of the filter capacitor at the rectifiers to the positive output terminal.

OBJECTIVE 1: Start at the negative output terminal TB1-7, in section 10, back to post 18 section 8, through R12 and X5 to post 2 section 5, through the normally closed contact of CB1, through the coil of CB1 to post 1, and from post 1 up to the negative side of the filter capacitor, C3.

OBJECTIVE 2: Starting at the positive terminal, TB1-6, section 10, down and straight over to the positive terminal of the C3 filter capacitor.

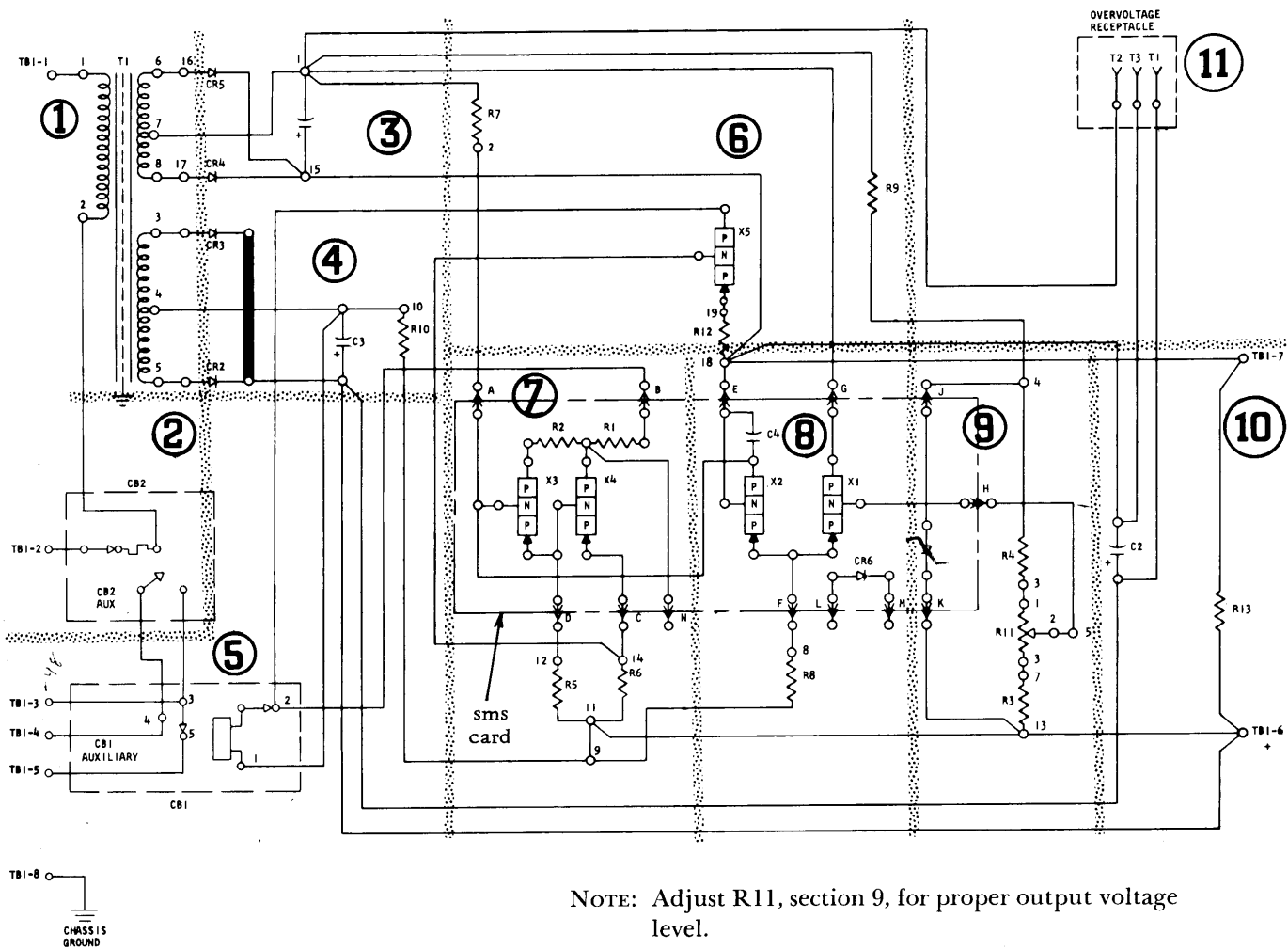


FIGURE 23. TYPICAL SERIES-REGULATED SMS POWER SUPPLY

TABLE OF AVAILABLE 60-CYCLE SMS POWER SUPPLIES

<i>Voltage</i>	<i>Current</i>	<i>Reg. To:</i>	<i>Comment</i>
± 3v	5a	±25%	Marginal Check Power Supply
± 6v	2a	± 2%	
± 6v	4a	± 2%	
± 6v	8a	± 2%	
± 6v	12a	± 2%	
± 6v	16a	± 2%	
± 6v	20a	± 2%	
±12v	8a	± 8%	No-Series Regulator
±12v	2a	± 2%	Can be referenced to either ground or -6 volts depending on which differential amplifier card is used.
±12v	4a	± 2%	
±12v	8a	± 2%	
±12v	12a	± 2%	
±12v	16a	± 2%	
±12v	20a	± 2%	
-20v	6a	± 8%	For use in Relay Circuits
-20v	15a	± 8%	
+30v	2a	± 2%	
+30v	4a	± 2%	
+30v	10a	± 2%	
+30v	4a (S*)	± 2%	Special supply for core storage has external voltage adjustment control
-36v	2a	± 2%	
-36v	4a	± 2%	
-36v	8a	± 2%	
+48v	6a	±10%	Non-standard voltage provided for existing 48-volt relay circuits
+60v	6a (S*)	± 2%	Has external voltage adjustment control

*Power Supplies not suitable for SMS Mounting*

± 3v	5a	±25%	Portable Marginal Check Power Supply
+60v	10a	± 2%	IBM 1403 Printer Supply

\* (S) - Storage